


# BRASSM (Maestro™ Brass Master™ Replica) Stage 2 Wiring

Version 2009 November 20

Copyright 2009 JD Sleep

*Permission refused for posting/serving this file from any site other than [www.generalguitargadgets.com](http://www.generalguitargadgets.com)*

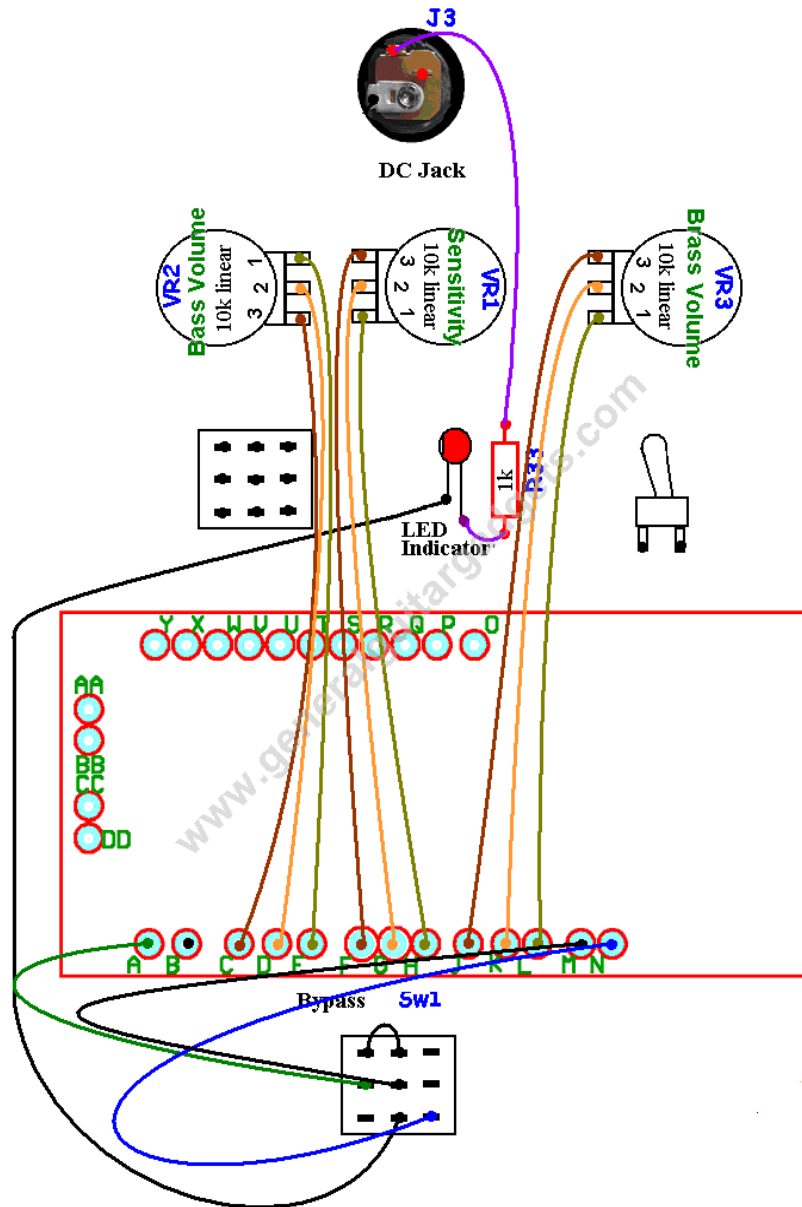*Trademarks are property of their owners*



Stage 2 wiring: Wire the potentiometers from the pads on the lower side of the PCB. Run the wires over top of the PCB. Wire the input and output and ground from the PCB to the Bypass foot switch. Leave lots of room on the wires to the foot switch so that the PCB can be lifted up and the underside of the PCB can be serviced later if needed.