

FolkUrban Music Jawari Project

Version 2007August13

Copyright 2006 JD Sleep

Permission refused for posting/serving this file from any site other than www.generalguitargadgets.com

This project is from the FolkUrban Music site

(<http://www.geocities.com/tpe123/folkurban/>)

the schematic is here:

<http://www.geocities.com/tpe123/folkurban/fuzz/snippets.html>

This will give your guitar a sitar type sound as in the sound samples on the "snippets" site.
Thanks to Dean Hazelwanter for the layout.

Bill of Materials

Resistors (1/4 watt rating)

1 – 1k

1 – 100k

1 - 1M

Pots (1/4 watt or higher rating)

1 – 10k linear

Transistors

1 – J201 or other JFET transistor.

Capacitors (minimum 16 volt rating)

1 – 0.1uF film

1 – 1uF aluminum electrolytic

1 – 22uF aluminum electrolytic

Other

1- 42TM018 or 42TL218

2 – 1N34A diode

1 – 1N914 or 1N4148

1 – 3PDT or DPDT heavy duty foot switch
(bypass)


1 – mono quarter inch jack

1 – stereo quarter inch jack

9v battery snaps & holder and/or DC jack,
knobs, Copper-clad board, etchant, or
perfboard

24 gauge stranded wire

Enclosure

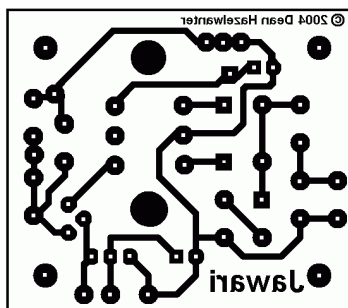

Size 4.7cm x 4cm

FolkUrban Music Jawari Project

Version 2007August13

Copyright 2006 JD Sleep

Permission refused for posting/serving this file from any site other than www.generalguitargadgets.com

